

LECTURE NOTES

On

Circuit & Network Theory

On

3rd Semester of Electrical Engineering Branch

Prepared by
ANKITA GURU (PTGF Electrical)

ch-2Voltage

- energy is required for the movement of charge from one point to another point. The energy required to move a positive charge from one point to another is known as voltage.
- even if there is no change between two points, voltage can still exist.
- voltage is given by

$$V = \frac{\text{energy required}}{\text{charge}}$$

$$V = W/Q$$

$$\text{unit} = \frac{\text{Joule}}{\text{Coulomb}} = \text{Volt} = V$$

Current

- It is the movement of electric charges along a definite path.

- unit of current is ampere (A)

Power

- it is the work done per unit time

$$P = \frac{\text{work done}}{\text{time}} = W/t$$

$$P = \frac{\text{work}}{\text{charge}} \times \frac{\text{charge}}{\text{time}}$$

$$P = V \times I$$

- unit of power is watt.

Energy

- It is defined as the power consumed in a given time.
- $w = P \times t$
 Joule
- unit of ~~power~~ energy is joule/watt second when
high

Resistance

- The property by which current is opposed to flow in an element is known as resistance.

Ohm's law

It states that under constant temperature in a conductor voltage is directly proportional to current

$$V \propto I$$
$$\Rightarrow V = IR$$

where 'R' = Resistance

Proportionality constant known as resistance of conductor

unit - Ω ohm

Inductance (L)

- Voltage is induced in a conductor when placed in a varying magnetic field.
- Induced voltage $\propto$ time rate of ~~current~~ change of current
$$e \propto \frac{dI}{dt}$$
$$e = L \frac{dI}{dt}$$

where 'L' Inductance

unit Henry (H, m)

Capacitance (F)

A capacitance is a physical device which when Polarized by an electric field by applying a suitable voltage stores energy in the form of charge separation.

The capability of a capacitor to store energy or charge is measure in form of capacitance.

$$C = q/v = \frac{\text{coulomb}}{\text{volt}}$$

unit - Faraday (F)

Bilateral & unilateral elements

Bilateral

Bilateral element conducts equally well in either condition.

ex - Resistor, Inductor

unilateral

when the current voltage relation are different for the 2 direction of current flow is known as unilateral element.

ex - diode

linear & non-linear element

when the current & voltage relation in an element can be stimulated by a linear equation either algebraic differential or Integral type the element is said to be linear element.

ex - ~~resistor~~ capacitor
resistor

Non-linear

when the current & voltage relationship in an element cannot be stimulated by a linear equation the element is said to be non-linear element.

Active & Passive element

- Active element produces energy in the form of voltage or current
ex: capacitor.

- Passive element stores energy in the form of voltage or current.

ex: resistor.

Resistivity

21 sep

Resistance of an element depends upon the length area or cross section directly and Inversely respectively

$$R \propto \frac{l}{A}$$

$$R = \rho \int \frac{l}{A}$$

$$\rho = \frac{RA}{l}$$

where ρ = proportionality constant known as Resistivity of the conductor.

unit of Resistivity is $-\Omega\text{-m}$

Conductance (G)

It is opposite of resistance that is that is the property of an element to allow current to pass through it

unit = mho (Ω^{-1})


Conductivity (σ)

$$\sigma = \frac{1}{\rho} = \frac{l}{RA}$$

unit = mho/m.s

Kirchhoff's current law (KCL)

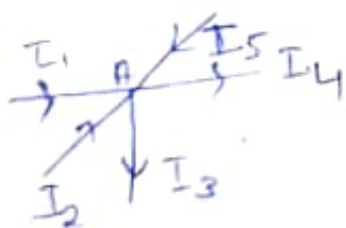If there is node or point where Incoming & outgoing current are present then Incoming current will always be equal to the summation of outgoing current.



Incoming current = I_1, I_2, I_5

outgoing current = I_3, I_4

according to KCL Σ Summation of In

Incoming current = Summation of outgoing

$$I_1 + I_2 + I_5 = I_3 + I_4$$